

# Operational Amplifier

# Operational Amplifier

Integrated circuit many stages of matched transistor amplifiers

Very high gain differential amplifier

High input impedance and low output impedance


Initially designed for mathematical operations: multiplication, division, addition, subtraction etc

$v_1$  - voltage at non-inverting input

$v_2$  - voltage at inverting input

$v$  - Output voltage

All are measured wrt ground

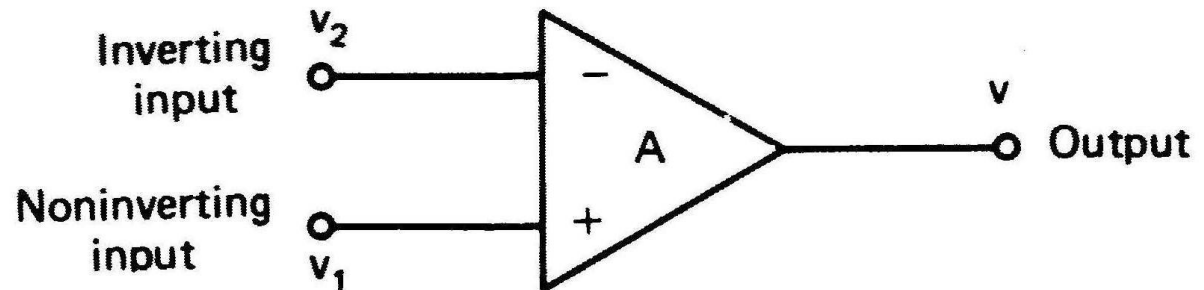




Output is amplification of difference at input terminals

# Operational Amplifier

Simple to use and understand as compared to transistors. Large number of applications. Most popular is 741 (8 pin dip).

Can be used in many modes

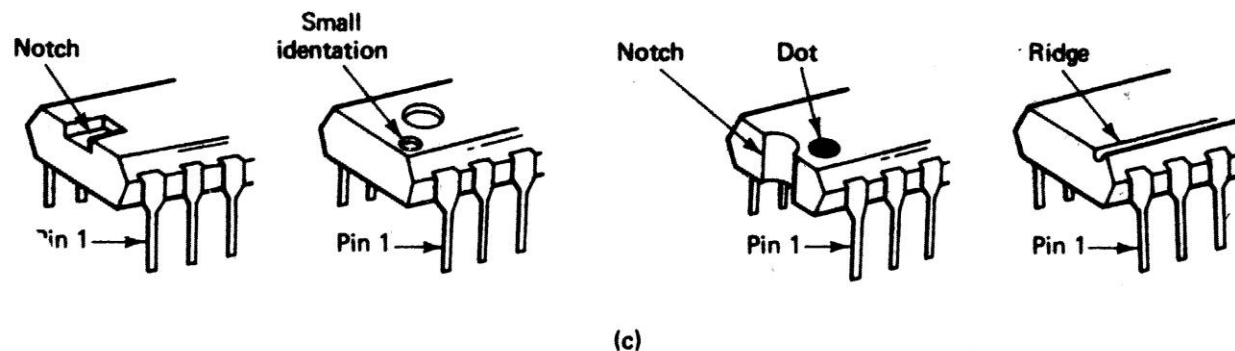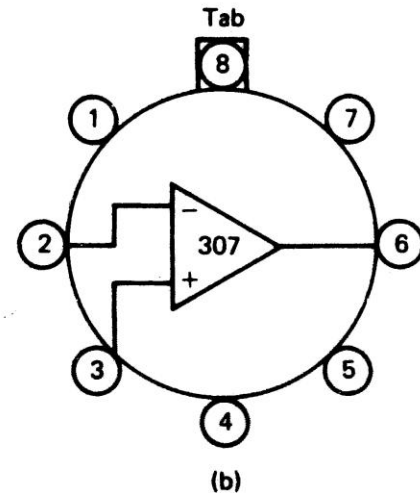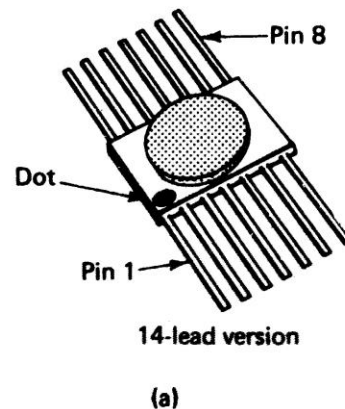- Differential
- Single ended
- Open loop
- Feed back



# Operational Amplifier

## Pin assignment


Generally in circuit diagram connection are pointed to pin number 2, 3, 4, 7 and 6.

Pin 2 & 3 are input

Pin 4 & 7 are power supply

Pin 6 is output


Pin 1 & 5 for offset null

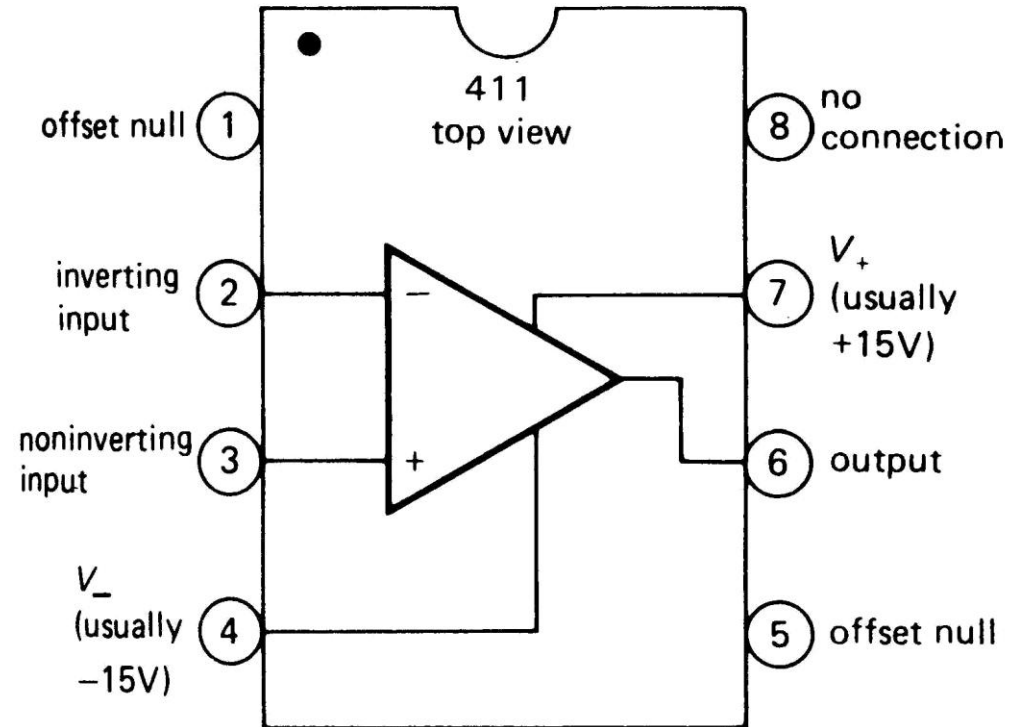

# Operational Amplifier

*Common mode rejection ratio:* Ratio of common mode differential voltage gain  $A_d$  to common mode voltage gain  $A_{cm}$ .

$$\text{CMRR} = \frac{A_d}{A_{cm}}$$

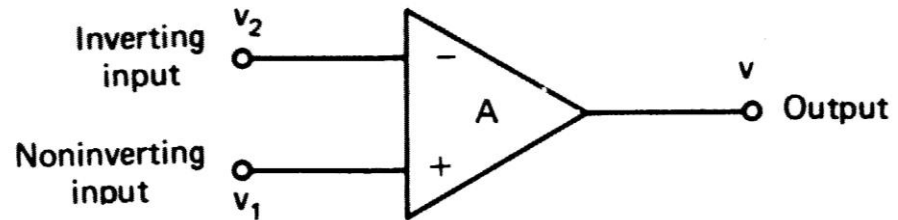

Generally  $A_d$  is very large compared to  $A_{cm}$  and CMRR is a very large number. Typically 90dB ~ 31.6 k Higher the number it is better. This quality is important when the OpAmp is used in differential mode. Helps in noise reduction. Generally noise is common to both the input terminals and the applied signal is voltage difference at the input terminals. For precision opamp it is as high as 120 dB.

# Operational Amplifier

*Large-signal voltage gain:* Ratio of output voltage to difference of input voltage. It is very high 20 k. It means that 0.05 mV differential voltage at input will give one volt output.

*Output voltage swing:* This is the saturation voltage of output in positive and negative range. This will always be less than supply voltage, generally 1 to 2 volts. Opamp with rail to rail output are also available.

*Output resistance :* Equivalent resistance at output i.e. measured between output terminal and ground. It is ~ 75 ohms.

*Gain bandwidth product :* The bandwidth of the op-amp when the voltage gain is one. This can be obtained from open loop voltage gain and frequency characteristics.

*Slew rate :* Maximum rate of change of output volt per second, important for high frequency signal. V/  $\mu$ S This is a measure of how rapidly output will change in response to input signal. Perfect square wave is not possible.

# Operational Amplifier

## Ideal op-amp


- Infinite voltage gain
- Infinite input resistance - no loading on source
- Zero output resistance - so that output can drive any number of devices
- Zero output voltage when input voltage is zero
- Infinite bandwidth
- Infinite CMRR
- Infinite slew rate

For practical opamps and practical use many of the characteristic can be approximated to above mentioned characteristics.



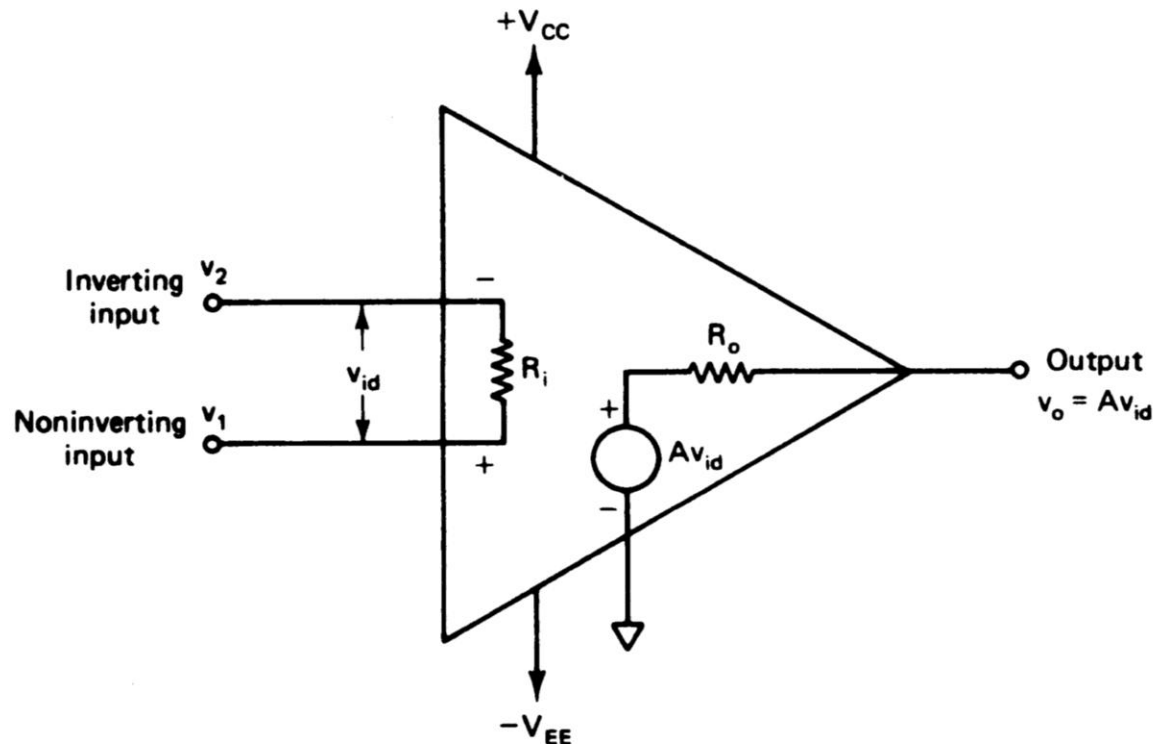
# Equivalent circuit of an op-amp

Equivalent circuit is shown using input resistance, output resistance, and open loop gain. Input resistance will load the source and output resistance will drive the output.


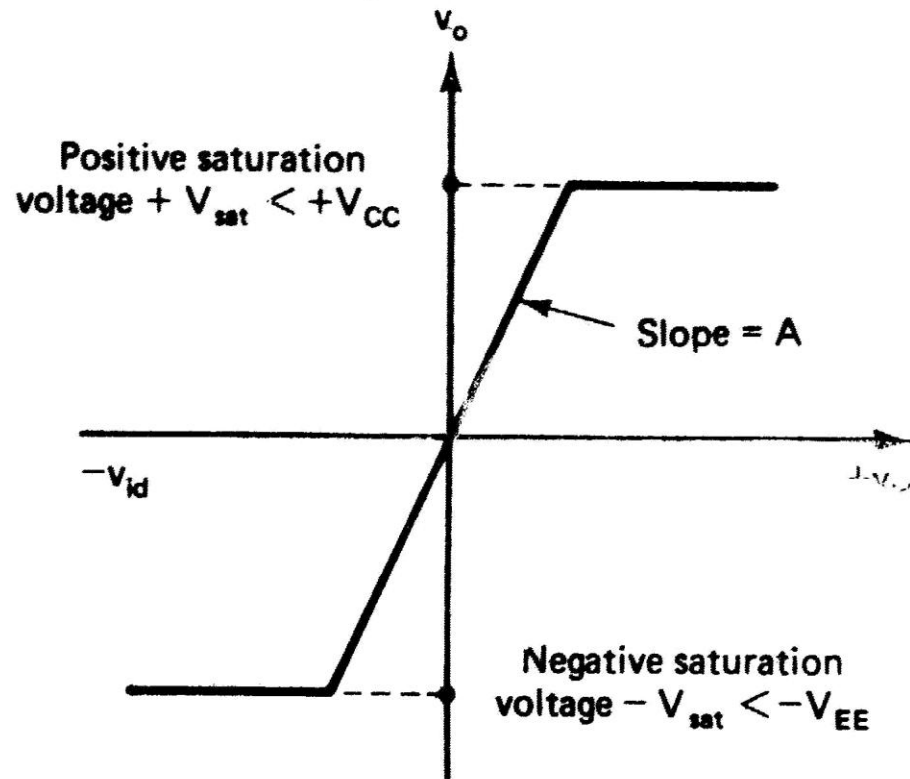
# Operational Amplifier

Ideal Voltage transfer curve : Output voltage cannot exceed the positive and negative saturation voltages. Offset voltage is zero. Slope is generally very large (almost vertical). Amplifies the difference in input voltages not the individual voltages.




# Operational Amplifier

Open-loop op-amp configuration

No connection between output and input

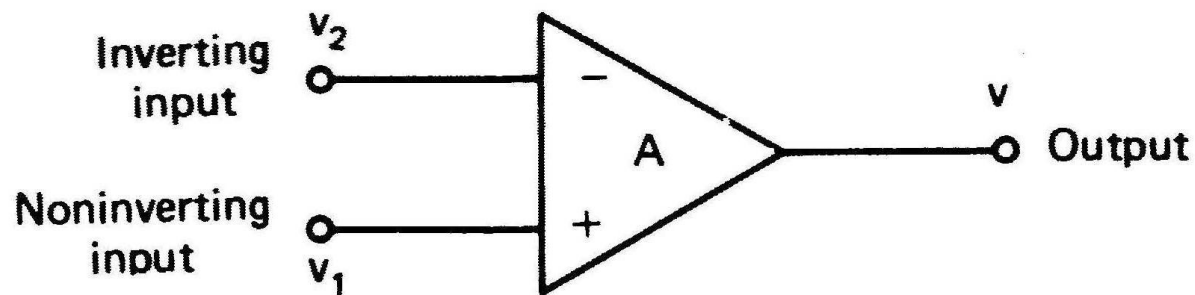- 1 Differential amplifier
- 2 Inverting amplifier
- 3 Noninverting amplifier



# Operational Amplifier


Non-inverting amplifier

Signal is applied to non-inverting (positive) terminal. Inverting terminal is grounded.

$v_o = A (v_1 - v_2) = A v_1$ , where  $A$  is open loop gain

Output is in phase with input, it will have same polarity as input.

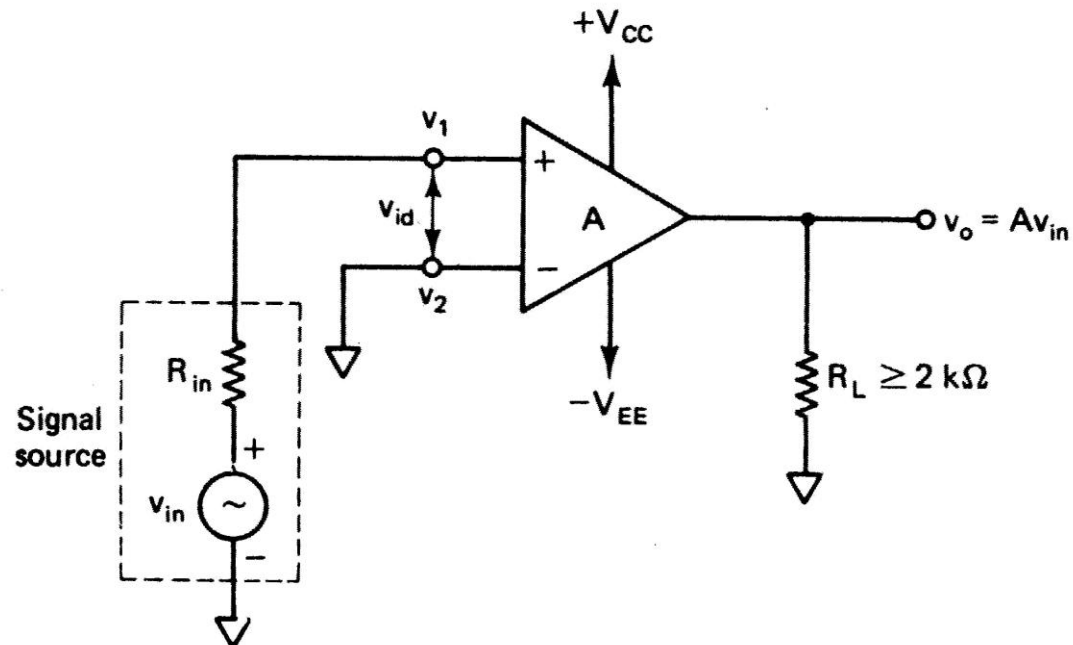In open loop configurations any input signal of few milli volts will saturate the output due to high open loop gain



# Operational Amplifier

Difference input voltage ideally zero



Opamp equation 
$$V_{id} = \frac{V_o}{A}$$

A is very large and ideally infinite.  $V_{id} = 0$

$v_1 = v_2$ , inverting and non-inverting terminal are at same voltage

Golden rule 1 : opamp will work in such a way that it will drives the two inputs to same level

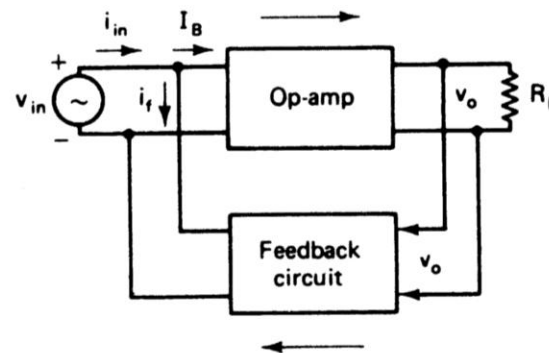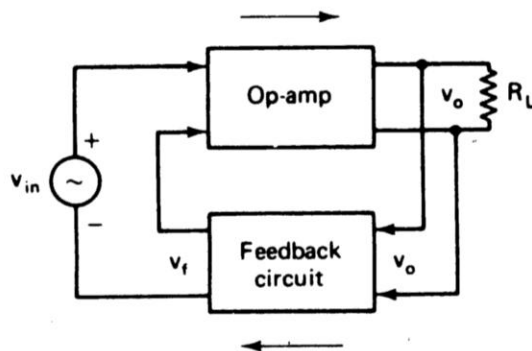Golden rule 2 : No current can flow into opamp




Using above two rules op-amp circuit analysis becomes easy

# Operational Amplifier

Voltage series feed back - Noninverting amplifier

Input - noninverting terminal (positive)

Feedback - inverting terminal

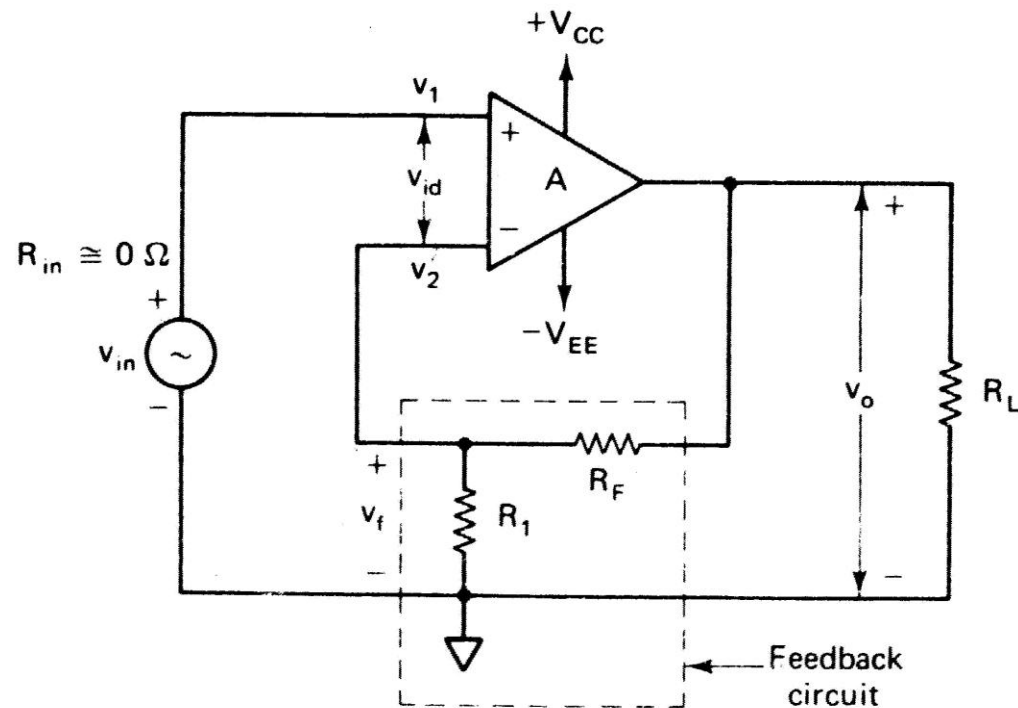

# Operational Amplifier


Closed loop voltage gain  $\mathbf{A_F} = \frac{\mathbf{V_o}}{\mathbf{V_{in}}}$

$$\mathbf{v_o} = \mathbf{A}(\mathbf{v_1} - \mathbf{v_2}) \quad \mathbf{v_1} = \mathbf{v_{in}} \quad \mathbf{v_2} = \mathbf{v_f} = \frac{\mathbf{R_1 v_o}}{\mathbf{R_1 + R_F}}$$

$$\mathbf{v_o} = \frac{\mathbf{A(R_1 + R_F)v_{in}}}{\mathbf{R_1 + R_F + AR_1}}$$

$$\mathbf{A_F} = \frac{\mathbf{V_o}}{\mathbf{V_{in}}} = \frac{\mathbf{A(R_1 + R_F)}}{\mathbf{R_1 + R_F + AR_1}}$$

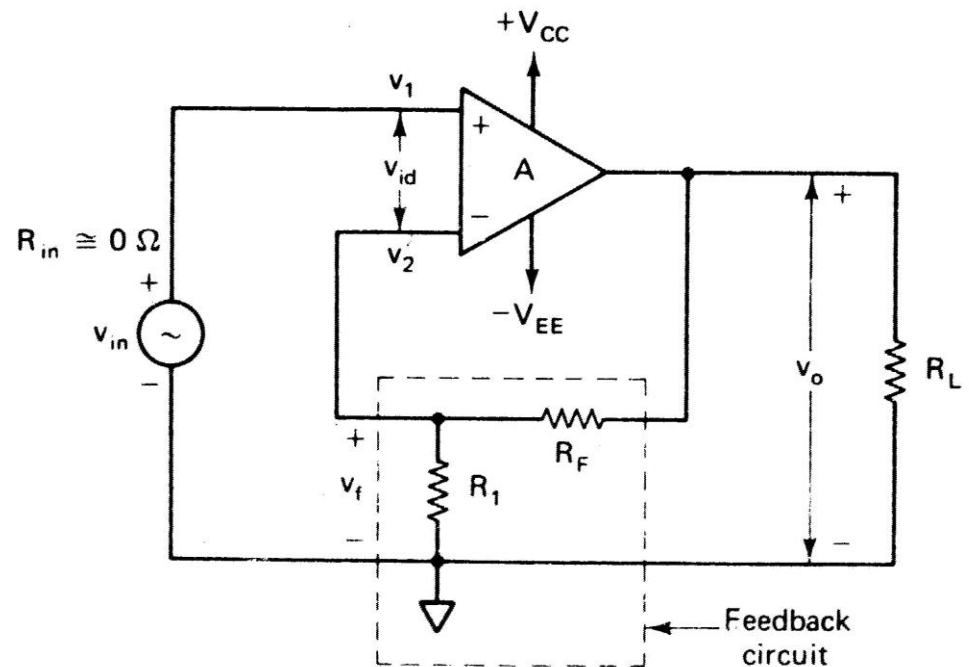Exact gain, involves open loop gain and generally not know correctly




# Operational Amplifier

Closed loop voltage gain  $A_F = \frac{V_0}{V_{in}} = \frac{A(R_1 + R_F)}{R_1 + R_F + AR_1}$  Exact

A is open loop gain  $AR_1 \gg R_1 + R_F$   $A_F = \frac{V_0}{V_{in}} = 1 + \frac{R_F}{R_1}$  Ideal

Gain is decided by two resistances:  $R_1$  and  $R_F$  independent of open loop gain

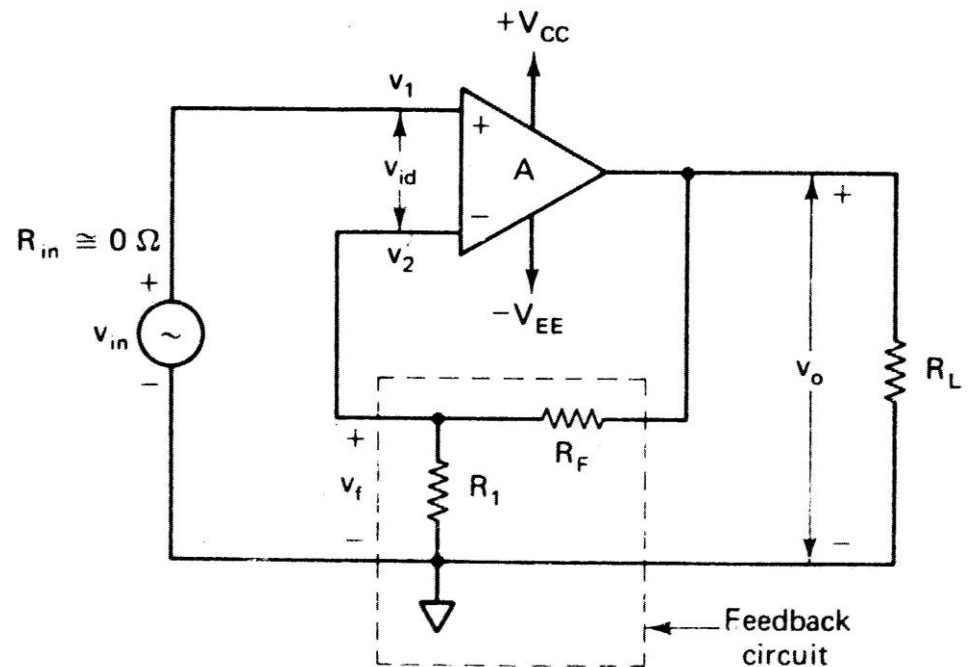As a general rule  $R_1$  and  $R_F$  should be less than 1 MΩ






# Operational Amplifier

Feedback gain  $\mathbf{B} = \frac{\mathbf{v}_f}{\mathbf{v}_o} = \frac{\mathbf{R}_1}{\mathbf{R}_1 + \mathbf{R}_F}$   $\mathbf{A}_F = \frac{1}{\mathbf{B}}$

$$\mathbf{A}_F = \frac{\mathbf{v}_o}{\mathbf{v}_{in}} = \frac{\mathbf{A}(\mathbf{R}_1 + \mathbf{R}_F)}{\mathbf{R}_1 + \mathbf{R}_F + \mathbf{A}\mathbf{R}_1} \quad \mathbf{A}_F = \frac{\mathbf{v}_o}{\mathbf{v}_{in}} = \frac{\mathbf{A}(\mathbf{R}_1 + \mathbf{R}_F)/(\mathbf{R}_1 + \mathbf{R}_F)}{(\mathbf{R}_1 + \mathbf{R}_F)/(\mathbf{R}_1 + \mathbf{R}_F) + \mathbf{A}\mathbf{R}_1/(\mathbf{R}_1 + \mathbf{R}_F)}$$

$$\mathbf{A}_F = \frac{\mathbf{A}}{1 + \mathbf{A}\mathbf{B}} \quad \text{Exact}$$
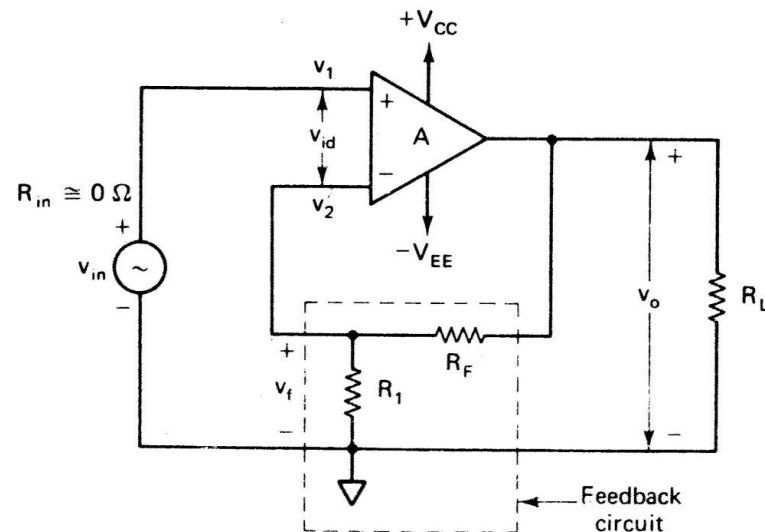
$$\mathbf{A}_F = \frac{\mathbf{v}_o}{\mathbf{v}_{in}} = \frac{1}{\mathbf{B}} \quad \text{Ideal}$$



# Operational Amplifier


Using Golden rule

a)  $v_1 = v_2$ , b) No current flows in to opamp

$$V_2 = \frac{R_1}{R_F + R_1} V_0$$

$$V_1 = V_{in} = V_2$$
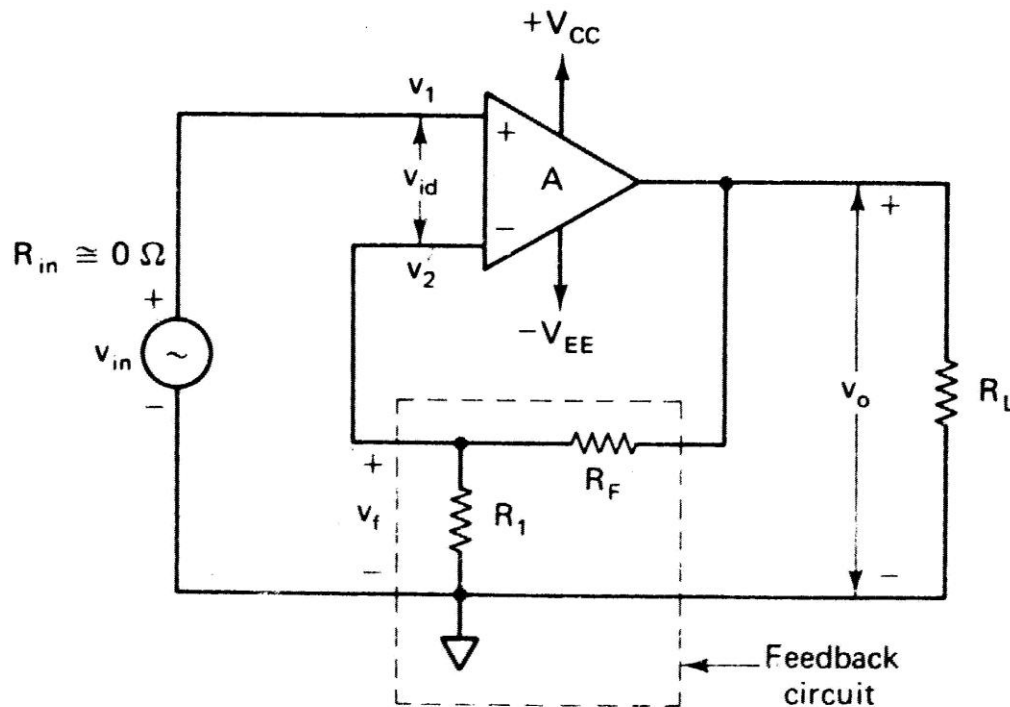
$$\frac{V_0}{V_{in}} = 1 + \frac{R_F}{R_1}$$



# Operational Amplifier

Input resistance with feed back

$$R_{iF} = R_i (1+AB)$$

$$B = 1/A_F$$

It means that input resistance in feed back is  $(1+AB)$  times than open loop input resistance  $R_i$ . It means that input resistance increases.

Output resistance with feed back

$$R_{oF} = R_o / (1+AB)$$


It means that output resistance in feed back is  $1/(1+AB)$  times open loop output resistance  $R_o$ . It means that output resistance in feed back is much smaller compared to open loop.

# Operational Amplifier
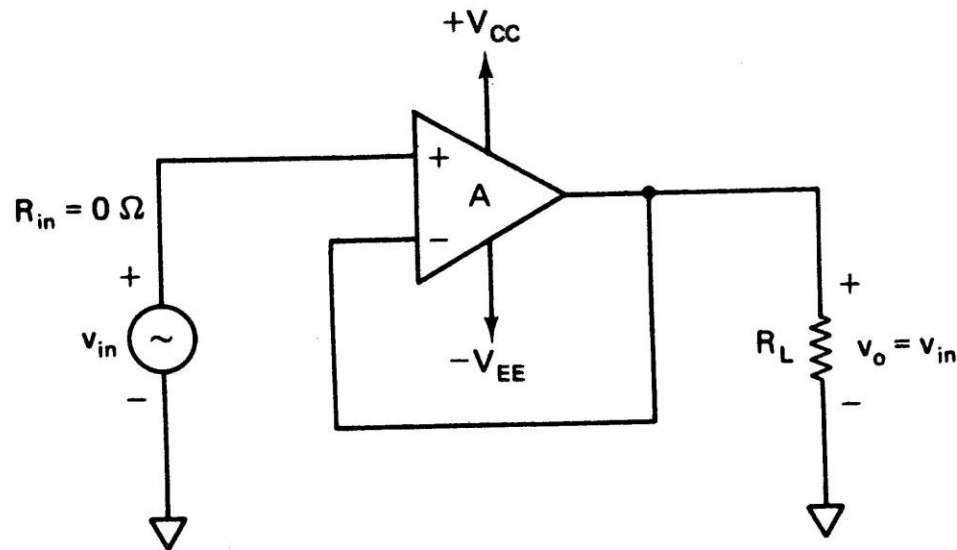
## Voltage follower

Lowest gain that can be obtained by a non-inverting amplifier is one, this configuration is called voltage follower. Output will follow the input.

Output is exactly equal to one and input resistance is very high



# Operational Amplifier



## Voltage shunt feedback amplifier

Non-inverting terminal is grounded. Signal to inverting terminal in series with resistance  $R_1$

$$\mathbf{i}_{\text{in}} = \mathbf{i}_F + \mathbf{I}_B \quad \mathbf{I}_B \approx 0 \quad \frac{\mathbf{v}_{\text{in}} - \mathbf{v}_2}{\mathbf{R}_1} = \frac{\mathbf{v}_2 - \mathbf{v}_o}{\mathbf{R}_F} \quad \mathbf{v}_1 - \mathbf{v}_2 = \frac{\mathbf{v}_o}{\mathbf{A}} \quad \mathbf{v}_2 = -\frac{\mathbf{v}_o}{\mathbf{A}}$$

$$\mathbf{A}_F = \frac{\mathbf{v}_o}{\mathbf{v}_{\text{in}}} = -\frac{\mathbf{A}\mathbf{R}_F}{\mathbf{R}_1 + \mathbf{R}_F + \mathbf{A}\mathbf{R}_1}$$
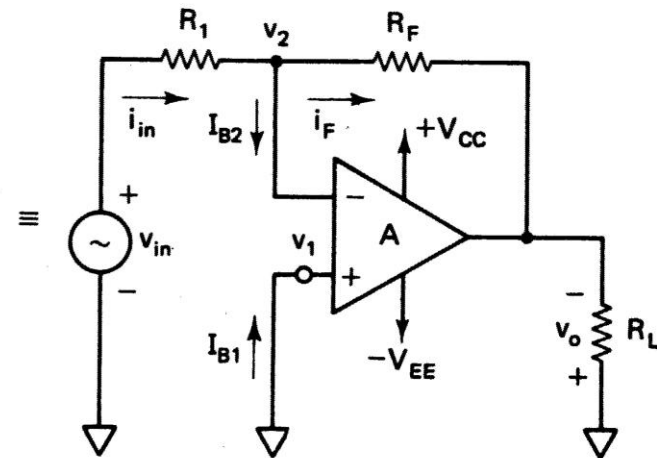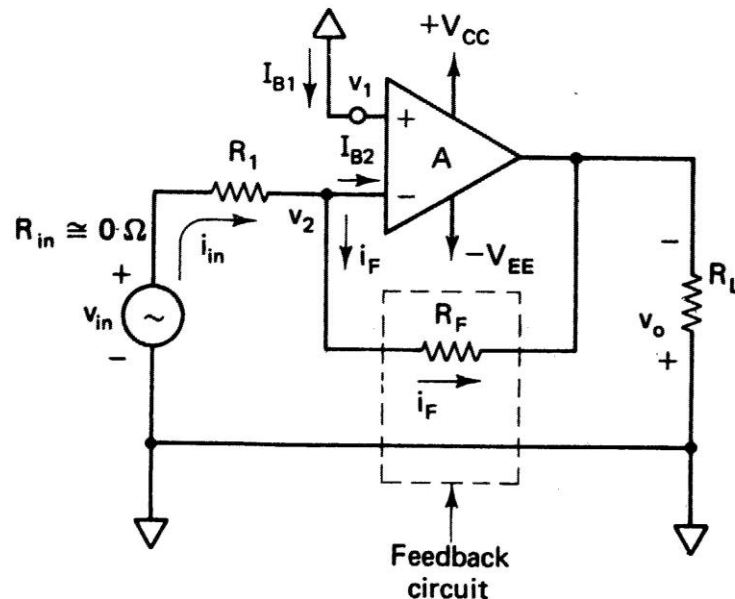
$$A_F = \frac{V_o}{V_{in}} = -\frac{R_F}{R_1}$$




# Operational Amplifier

## Voltage shunt feedback amplifier

$$A_F = \frac{V_0}{V_{in}} = -\frac{R_F}{R_1}$$

Gain less than one possible

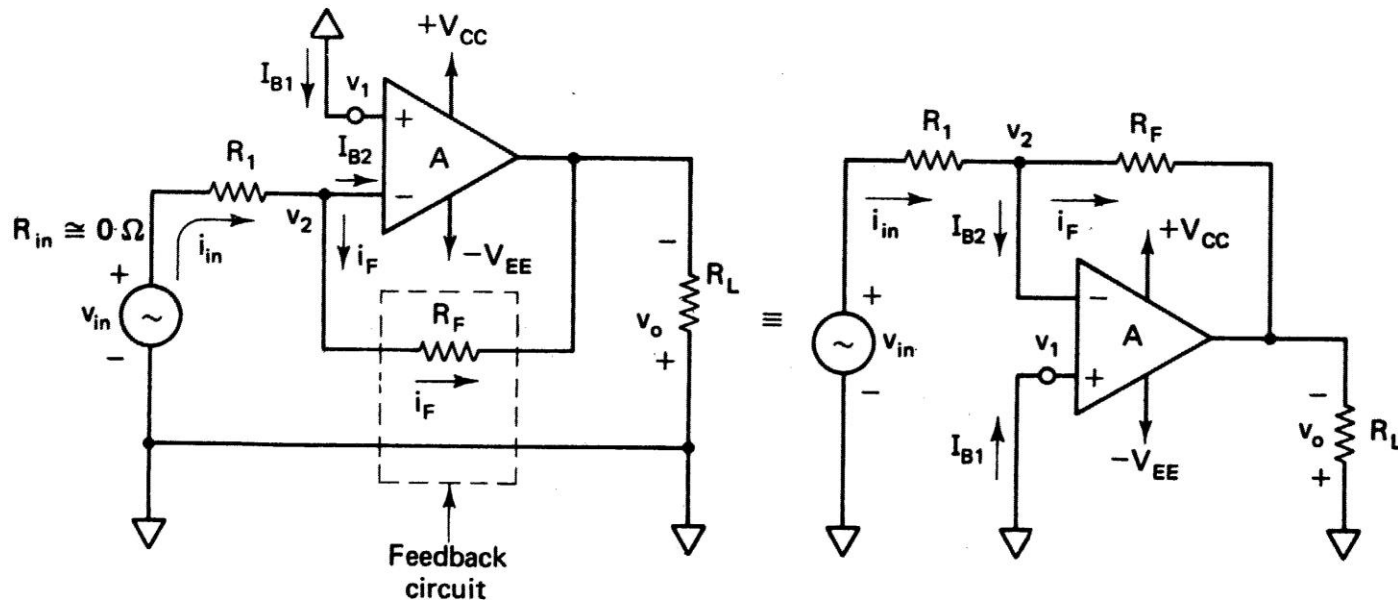Gain is set by two resistance  $R_1$  and  $R_F$  and independent of A



# Operational Amplifier

## Voltage shunt feedback amplifier

Using Golden rule


a)  $v_1 = v_2$ , b) No current flows in to opamp

$$A_F = \frac{V_0}{V_{in}} = -\frac{R_F}{R_1}$$

$$\frac{V_{in} - V_2}{R_1} = \frac{V_2 - V_0}{R_F}$$

$$V_1 = 0 = V_2$$
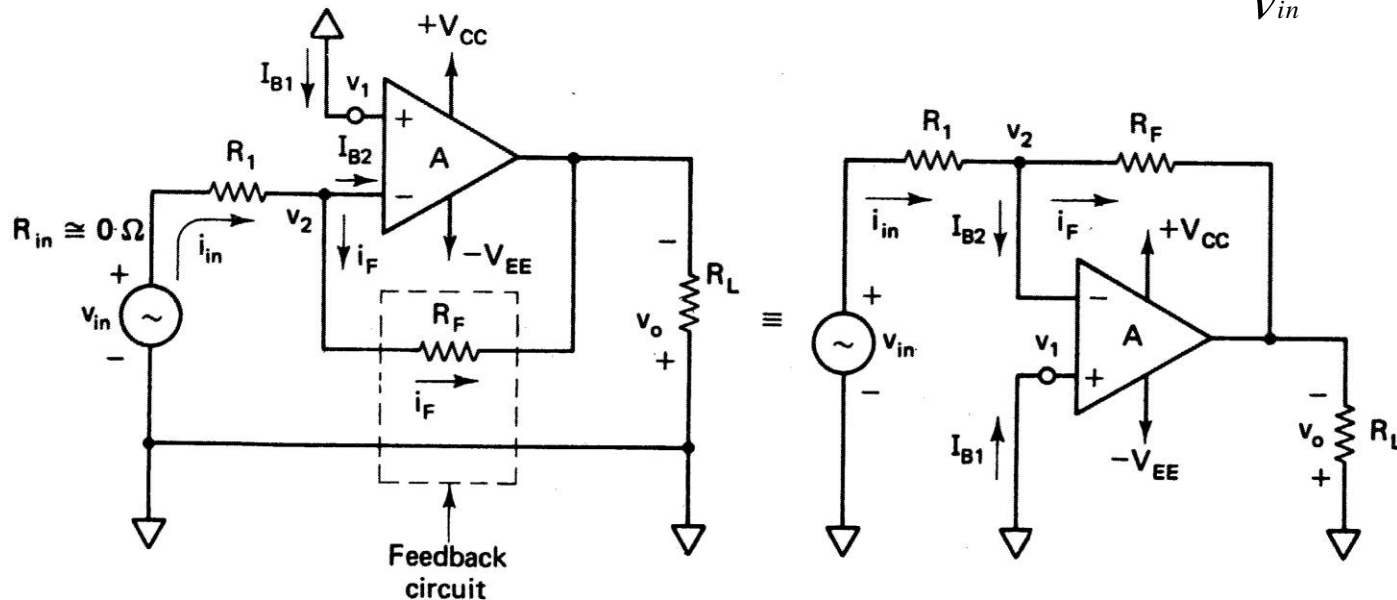
$$\frac{V_0}{V_{in}} = -\frac{R_F}{R_1}$$



# Operational Amplifier

Input resistance with feed back

$$R_{iF} = R_1$$

It means that input resistance in feed back is  $\sim$  resistance  $R_1$  much less compared to open loop input resistance  $R_i$ . Input resistance reduces considerably.

Output resistance with feed back

$$R_{oF} = R_o / (1 + AB)$$

It means that output resistance in feed back is  $1/(1+AB)$  times open loop output resistance  $R_o$ . Output resistance in feed back is much smaller compared to open loop. Same as non-inverting configuration.





# Operational Amplifier

## Current to voltage converter

$$V_o = -\frac{V_{in}}{R_1} R_F$$

If replace  $v_{in}$  and  $R_1$  combination by a current source, the output voltage will be proportional to current

## Sensing current from photodiodes

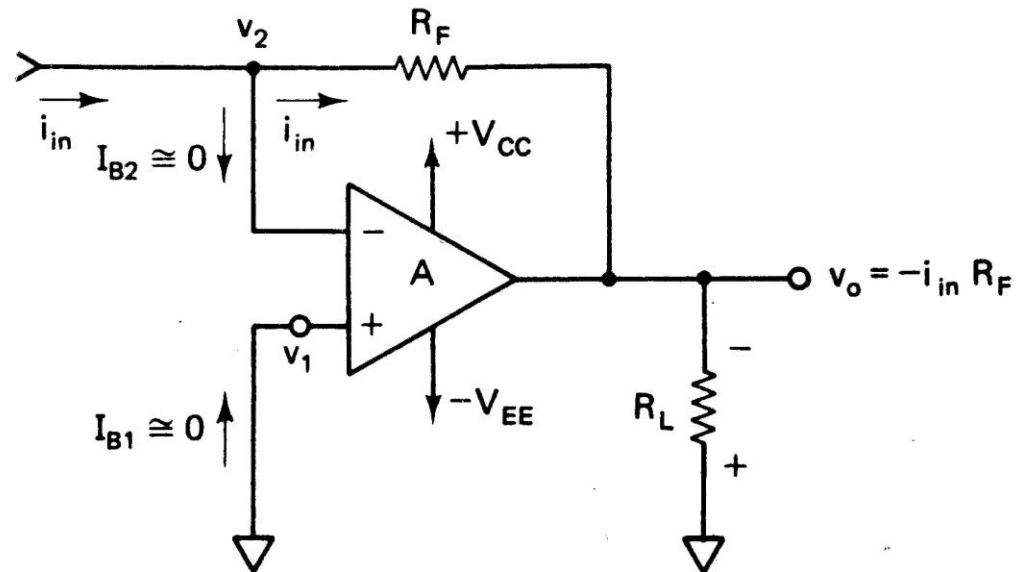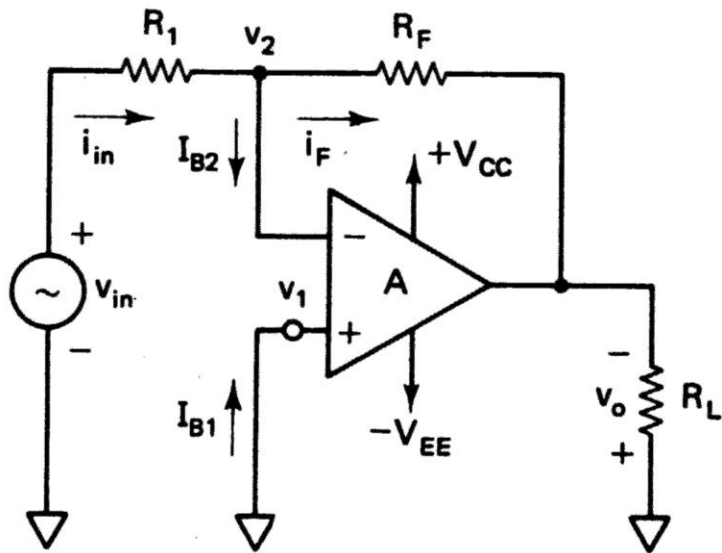

# Operational Amplifier


Summing amplifier - noninverting mode

Averaging of input signal

$$V_o = \left(1 + \frac{R_F}{R_1}\right) \frac{V_a + V_b + V_c}{3}$$

Summing, number of inputs =

$$\left(1 + \frac{R_F}{R_1}\right)$$

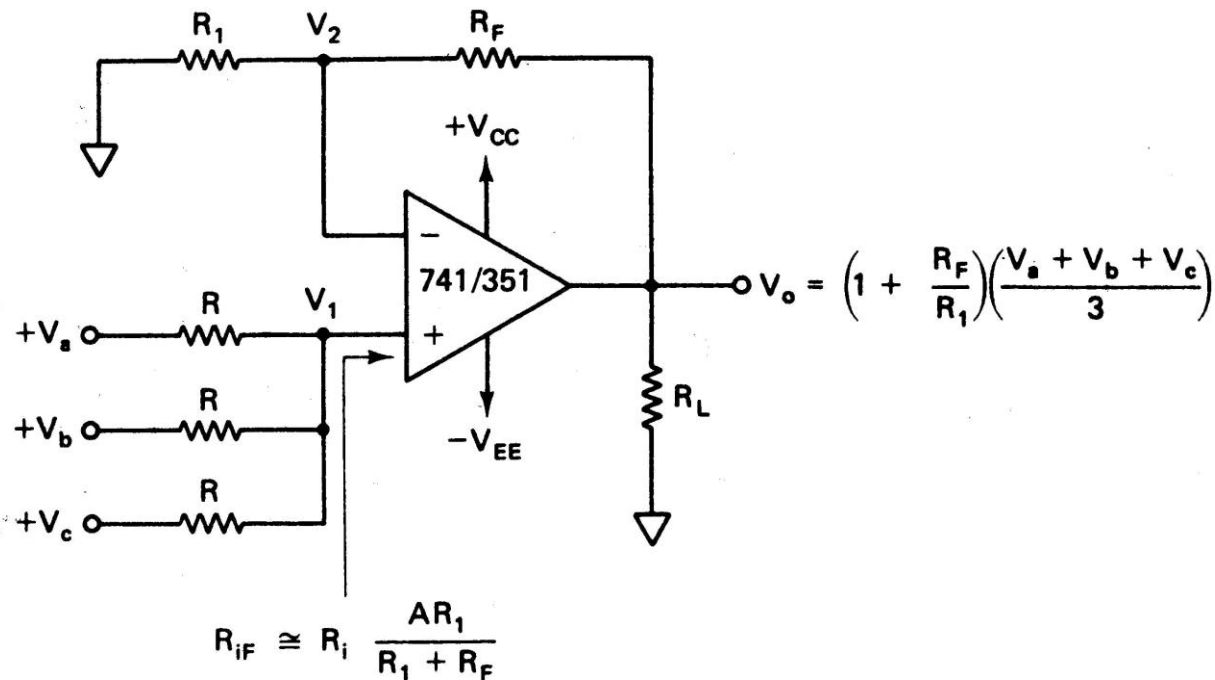


# Operational Amplifier

## Subtractor

Gain in inverting mode is 1

Gain in noninverting mode is 2

$$\text{Output, } V_o = V_b - V_a$$

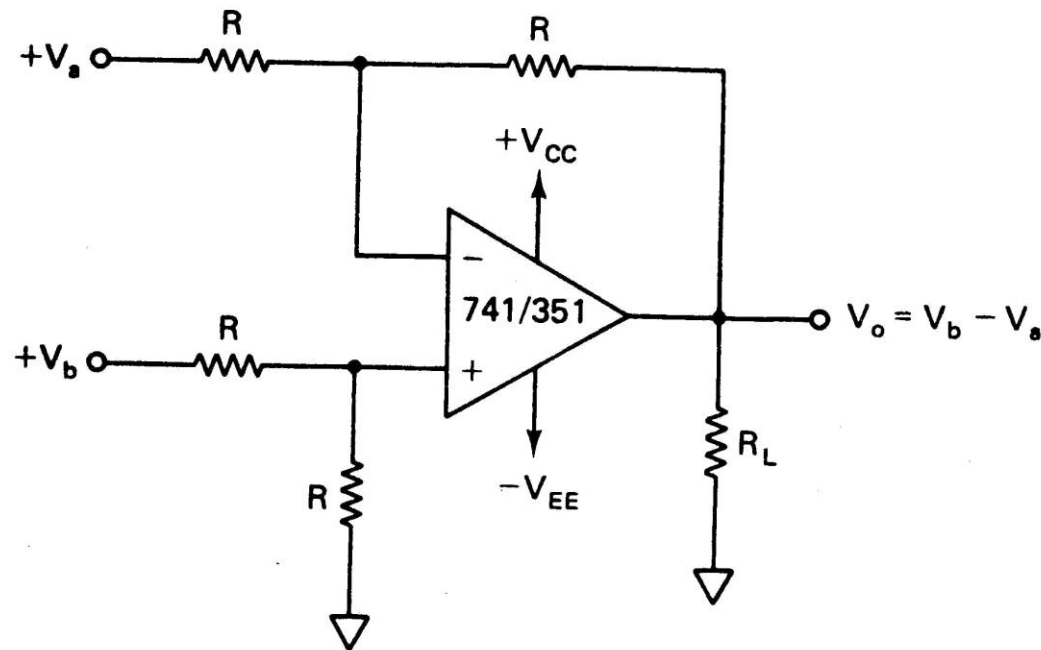

# Operational Amplifier


## Multi stage amplifier

$$v_o = A V_1 \text{ where } A = A_1 A_2 A_3$$

$A_1$  = Amplification of first amplifier

$A_2$  = Amplification of second amplifier

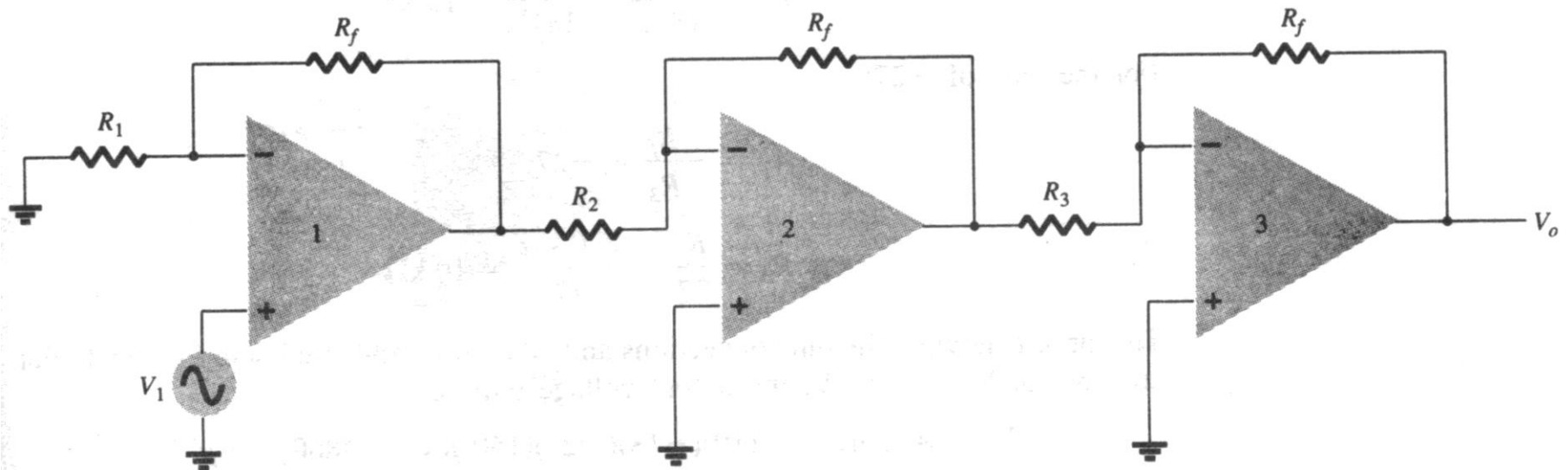
$A_3$  = Amplification of third amplifier


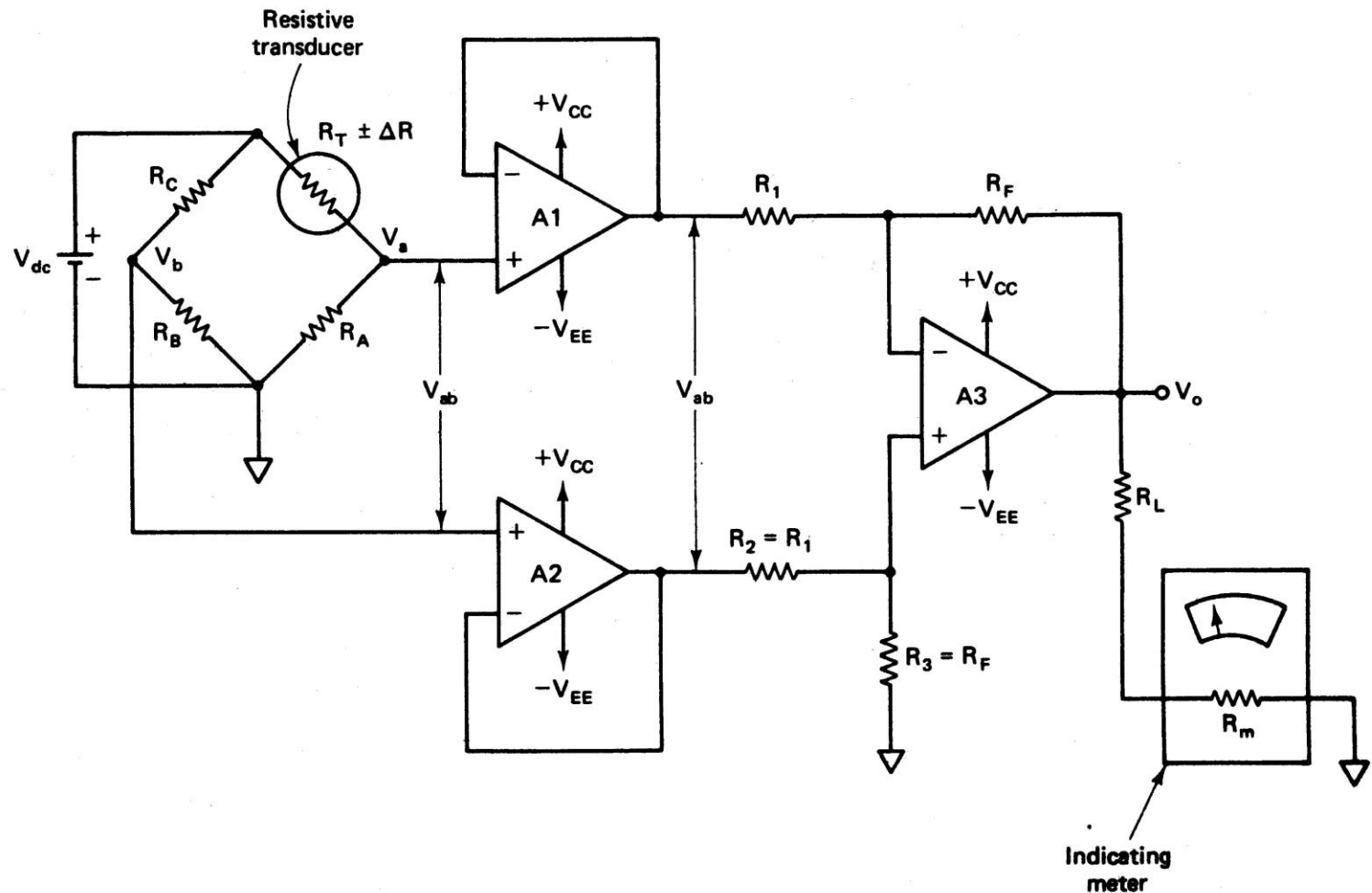
# Operational Amplifier

Instrumentation amplifier

Two voltage follower output given to a differential amplifier




# Operational Amplifier

Voltage to current converter

$$V_{id} = 0 ; V_f = V_{in}$$

$$i_o = \frac{V_f}{R_1} \quad i_o = \frac{V_{in}}{R_1}$$

Current is proportional to input voltage

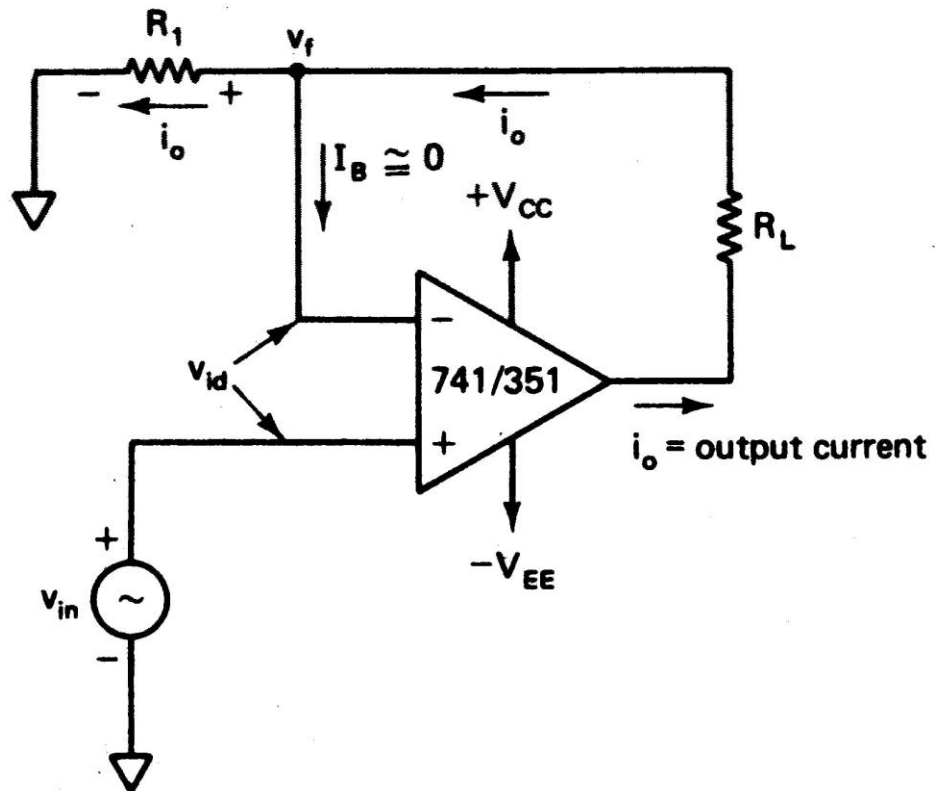

# Operational Amplifier

The integrator


The output is integral of the input signal is called integrator amplifier.

$$i_c = C \frac{dv_c}{dt}$$

$$\frac{V_{in} - V_2}{R_1} = C_F \frac{d}{dt} (V_2 - V_0)$$

$$\frac{V_{in}}{R_1} = C_F \frac{dV_0}{dt}$$
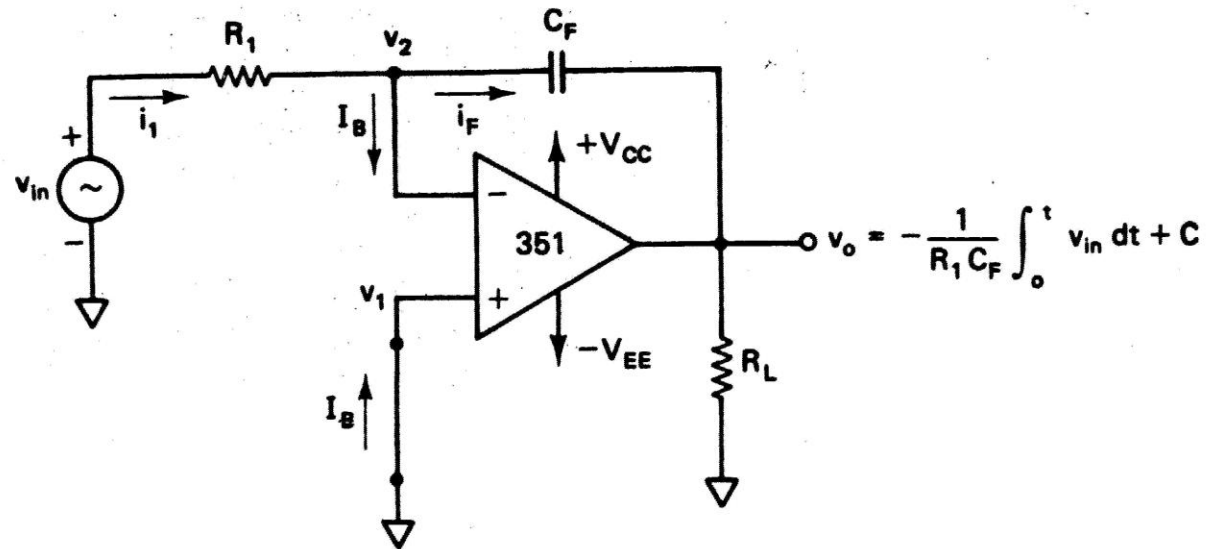
$$V_0 = -\frac{1}{C_F R_1} \int_0^t v_{in} dt + C$$






(a)


# Operational Amplifier
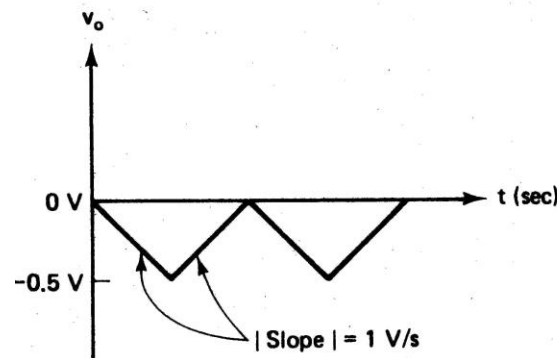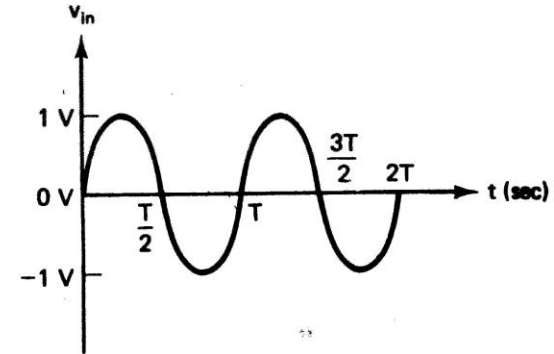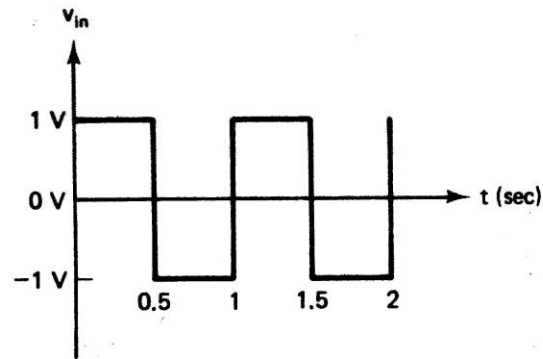
## The integrator

These are ideal waveforms  
integration errors due to  
constant bias is very  
common, which will increase  
linearly with time



(b)

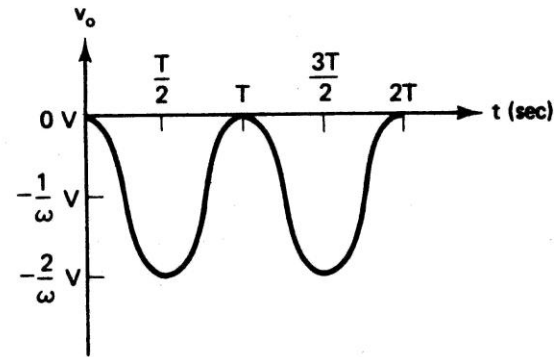

(c)



# Operational Amplifier


The differentiator

The output is differentiation of the input signal is called differentiator amplifier.

$$i_c = C \frac{dv_c}{dt}$$

$$C_F \frac{d}{dt} (v_{in} - V_2) = \frac{V_2 - V_0}{R_F}$$

$$V_0 = -R_F C_1 \frac{dV_{in}}{dt}$$

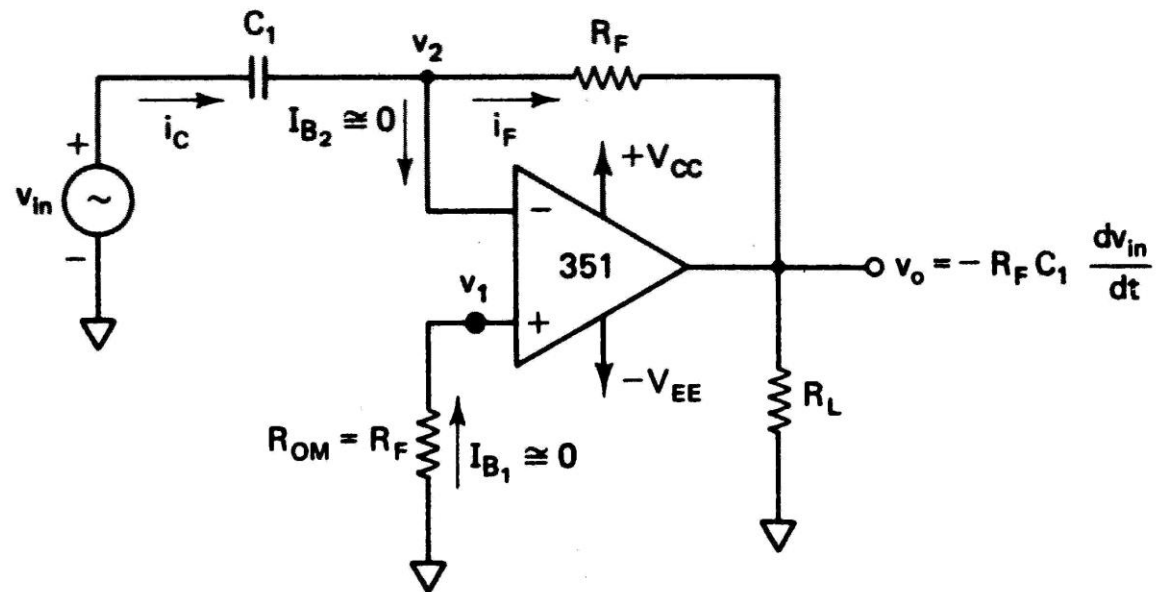




(a)

# Operational Amplifier

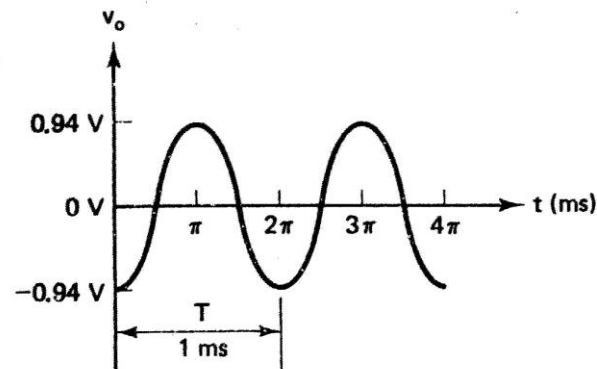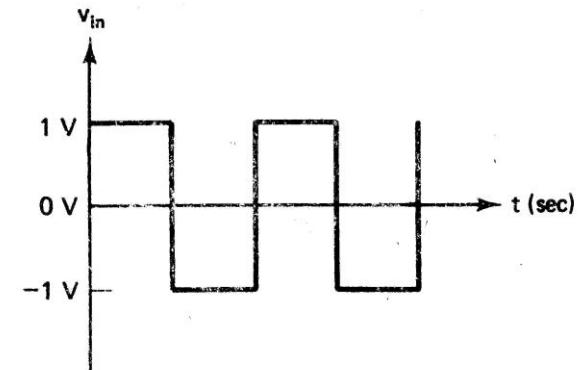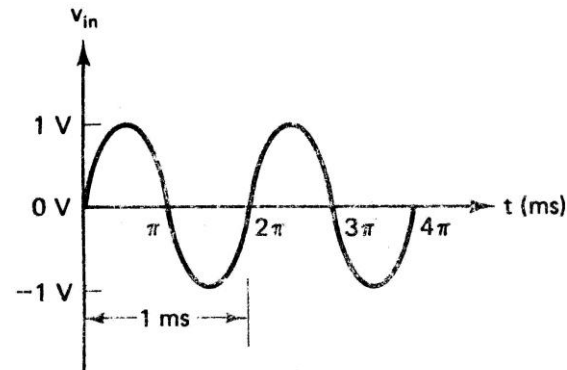
## The differentiator

Sine wave into a cosine wave

Spikes (high frequency noise) in signal is generally a problem in such circuits



(b)

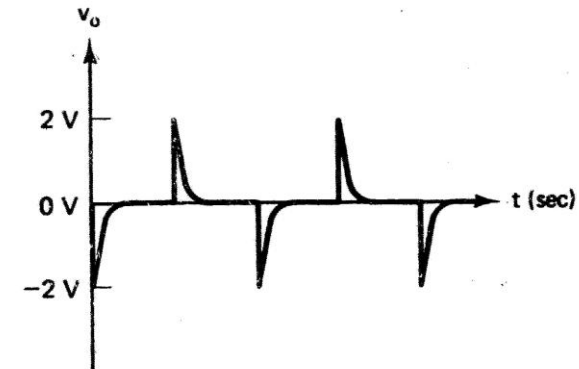

(c)

